



IEEE ENERGY CONVERSION CONGRESS & EXPO



Vancouver, Canada ☰ Oct. 10-14

Design Power Control Strategies of Grid-Forming Inverters for Microgrid Application

Jing Wang, Senior Research Engineer
National Renewable Energy Laboratory


10/12/2021



Background



- State-of-the-art grid-forming inverter control: PQ in grid-connected (current source) and VF in islanded mode (voltage source) ❌
- **Problem:** phase jump during microgrid transition operation
- **Solution:** use grid-forming control in both grid-connected and islanded mode
- **Problem:** grid-forming control controls system voltage rather than power.
- Objective: design power control strategy of grid-forming inverters for microgrid applications

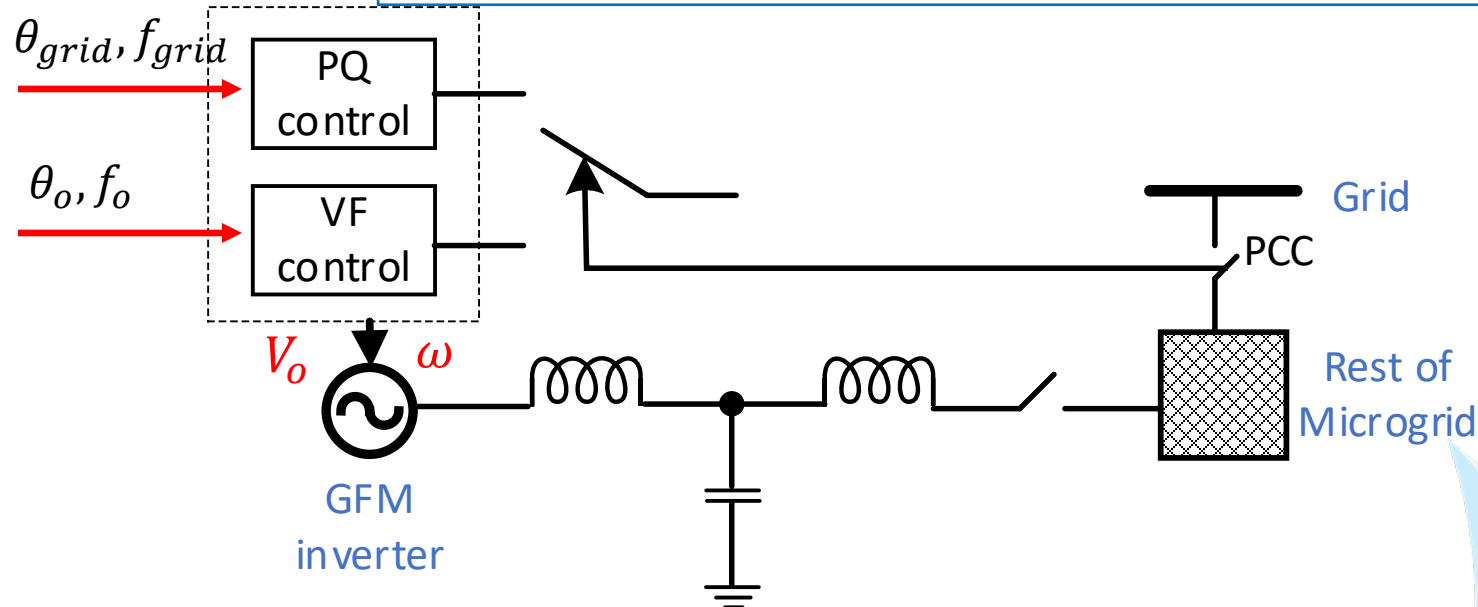How to control PQ via grid-forming control in grid-connected mode



Solution

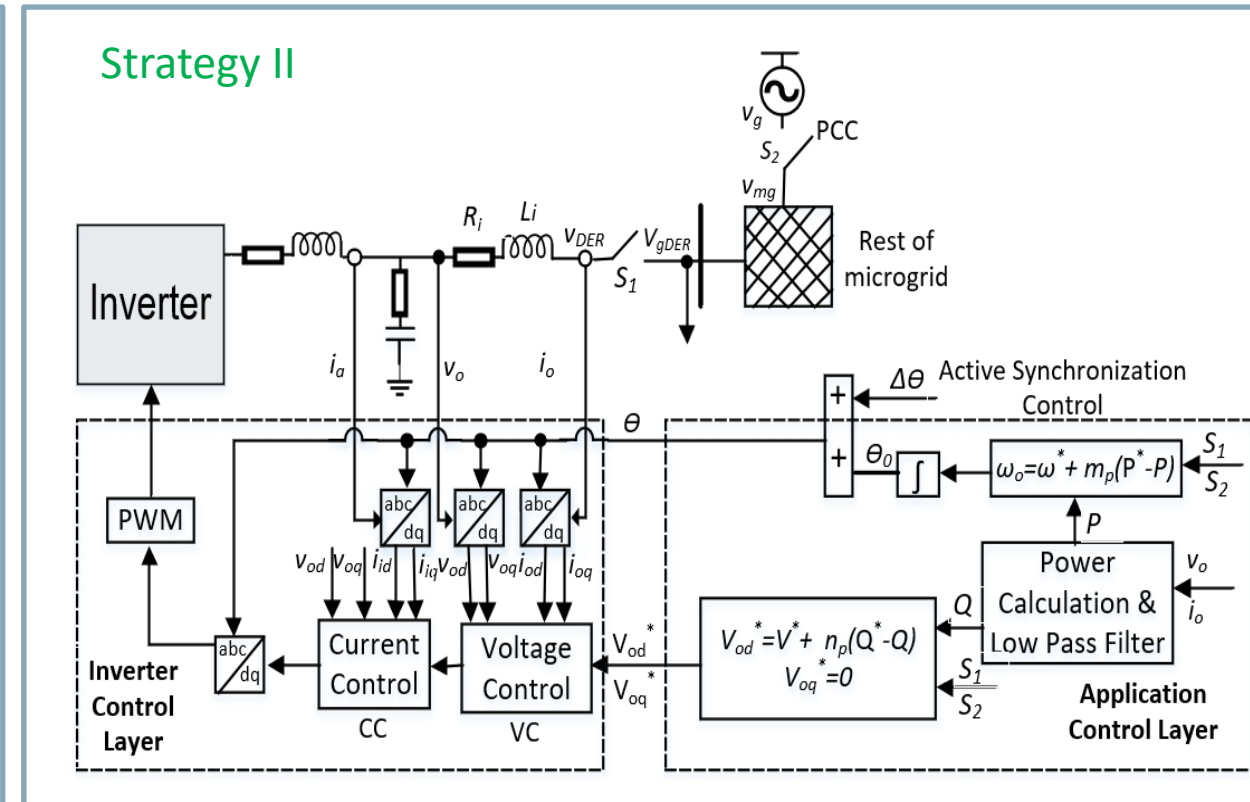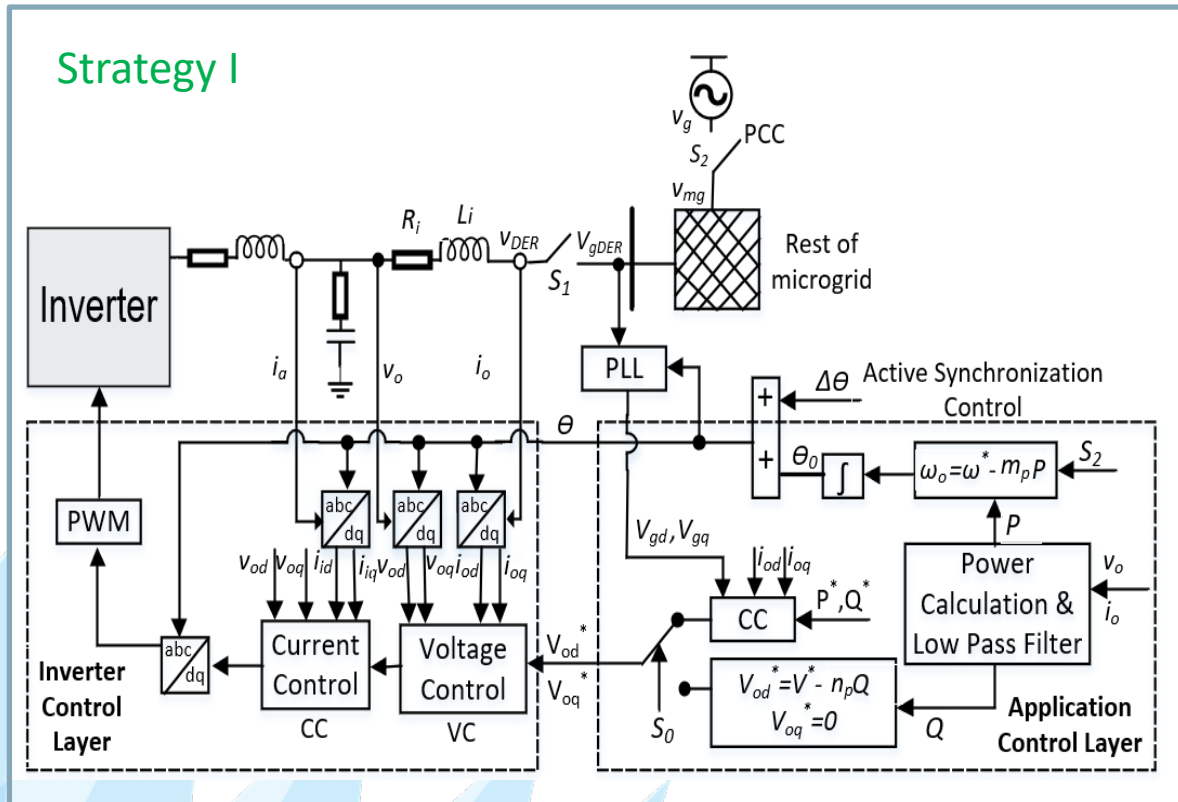- **Strategy I:** Current controller outer loop in grid-connected, and droop control in islanded mode
- **Strategy II:** Droop control in both grid-connected and islanded mode




Comparison of These Two Strategies

| Control Strategy | Startup | Grid-Connected | Islanded |
|------------------|---|--|---|
| Strategy I | $\omega_o = \omega^*$ $V_{od}^* = V^*$ $V_{oq}^* = 0$ | $\omega_o = \omega^*$ $V_{od}^* = V_{gd} + R_i i_{od}^* + K_{po}(i_{od}^* - i_{od}) - \omega_o L_i i_{oq}^*, i_{od}^* = \frac{2}{3} \frac{P^*}{V_{gd}}$ $V_{oq}^* = V_{gq} + R_i i_{oq}^* + K_{po}(i_{oq}^* - i_{oq}) + \omega_o L_i i_{od}^*, i_{oq}^* = -\frac{2}{3} \frac{Q^*}{V_{gd}}$ | $\omega_o = \omega^* - m_p P$ $V_{od}^* = V^* - n_p Q$ $V_{oq}^* = 0$ |
| Strategy II | $\omega_o = \omega^*$ $V_{od}^* = V^*$ $V_{oq}^* = 0$ | $\omega_o = \omega^* + m_p(P^* - P) \rightarrow \omega_o = \omega^*, P^* = P$ $V_{od}^* = V^* + n_p(Q^* - Q) \rightarrow V_{od}^* = V^* + (n_p + \frac{k_{np}}{s})(Q^* - Q)$ $V_{oq}^* = 0$ | $\omega_o = \omega^* - m_p P$ $V_{od}^* = V^* - n_p Q$ $V_{oq}^* = 0$ |

J Wang, B. Lundstrom, A. Bernstein, "Design of a non-pll grid-forming inverter for smooth microgrid transition operation," IEEE PESGM 2020.

$$i_{od} = \frac{1}{sL_i + R_i} (V_{od} - V_{gd} + \omega_o L_i i_{oq}), P = \frac{3}{2} V_{gd} i_{od}$$

$$i_{oq} = \frac{1}{sL_i + R_i} (V_{oq} - V_{gq} - \omega_o L_i i_{od}), Q = -\frac{3}{2} V_{og} i_{oq}$$

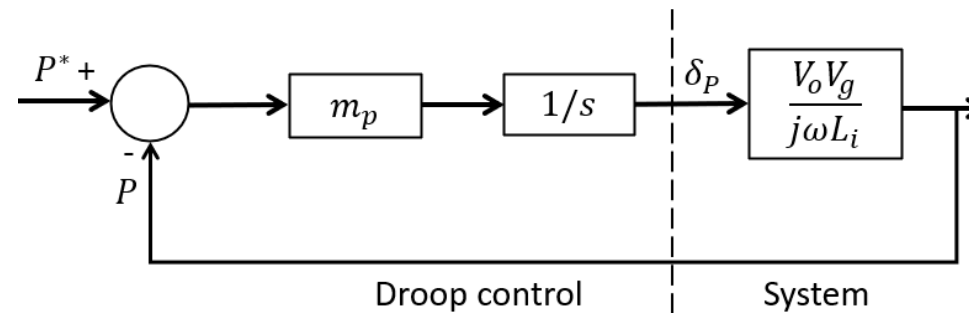

Strategy I: decouple the intrinsic power-angle characteristics

Strategy II: follow the power-angle characteristics

Different power-angle stability

Comparison of These Two Strategies

| Control Strategy | Startup | Grid-Connected | Islanded |
|------------------|---|--|---|
| Strategy I | $\omega_o = \omega^*$ $V_{od}^* = V^*$ $V_{oq}^* = 0$ | $\omega_o = \omega^*$ $V_{od}^* = V_{gd} + R_i i_{od}^* + K_{po}(i_{od}^* - i_{od}) - \omega_o L_i i_{oq}^*, i_{od}^* = \frac{2}{3} \frac{P^*}{V_{gd}}$ $V_{oq}^* = V_{gq} + R_i i_{oq}^* + K_{po}(i_{oq}^* - i_{oq}) + \omega_o L_i i_{od}^*, i_{oq}^* = -\frac{2}{3} \frac{Q^*}{V_{gd}}$ | $\omega_o = \omega^* - m_p P$ $V_{od}^* = V^* - n_p Q$ $V_{oq}^* = 0$ |
| Strategy II | $\omega_o = \omega^*$ $V_{od}^* = V^*$ $V_{oq}^* = 0$ | $\omega_o = \omega^* + m_p(P^* - P) \rightarrow \omega_o = \omega^*, P^* = P$ $V_{od}^* = V^* + n_p(Q^* - Q) \rightarrow V_{od}^* = V^* + (n_p + \frac{k_{ip}}{s})(Q^* - Q)$ $V_{oq}^* = 0$ | $\omega_o = \omega^* - m_p P$ $V_{od}^* = V^* - n_p Q$ $V_{oq}^* = 0$ |

Strategy I: $\omega^* - m_p P \rightarrow \omega^*$, v_{od}^*, v_{oq}^* has big step changes

Strategy II: $\omega^* - m_p P \rightarrow \omega^* + \Delta\omega$, v_{od}^* has small step change

$v_{oq}^* = 0$ all the time without change

- Both strategies are expected to have transients
- Strategy I should have better transients

$\omega^* \rightarrow \omega^* - m_p P$ for both strategies

Strategy I: v_{od}^*, v_{oq}^* has big step changes

Strategy II: v_{od}^* has small step change

$v_{oq}^* = 0$ all the time without change

Strategy II should have better transients

Comparison of These Two Strategies



Generated using the GFM inverter angle instead of its own angle

| Control Strategy | Grid-Connected | Power Tracking Performance |
|------------------|--|---|
| Strategy I | $\omega_o = \omega^*$ $V_{od}^* = V_{gd} + R_i i_{od}^* + K_{po}(i_{od}^* - i_{od}) - \omega_o L_i i_{oq}, i_{od}^* = \frac{2}{3} \frac{P^*}{V_{gd}}$ $V_{oq}^* = V_{gq} + R_i i_{oq}^* + K_{po}(i_{oq}^* - i_{oq}) + \omega_o L_i i_{od}, i_{oq}^* = -\frac{2}{3} \frac{Q^*}{V_{gd}}$ | $V_{gd} \approx V'_{gd}, V_{gq} \neq V'_{gq} = 0$ <ul style="list-style-type: none"> Active power tracking can be acceptable Reactive power tracking has discrepancy |
| Strategy II ✓ | $\omega_o = \omega^* + m_p(P^* - P) \rightarrow \omega_o = \omega^*, P^* = P$ $V_{od}^* = V^* + n_p(Q^* - Q) \rightarrow V_{od}^* = V^* + (n_p + \frac{k_{np}}{s})(Q^* - Q)$ $V_{oq}^* = 0$ | <ul style="list-style-type: none"> Active power must track P^* to reach steady-state frequency for stability Reactive power can track the Q^* because of PI control |

Strategy I: terminal voltage dependent


Strategy II: less dependent on the terminal voltage

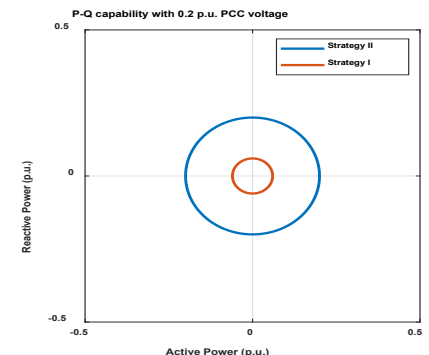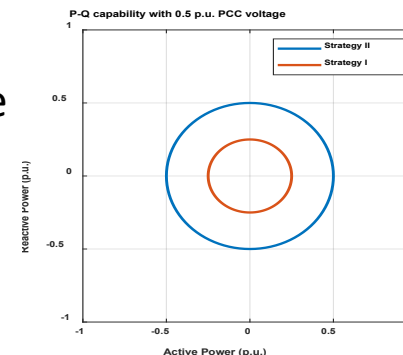Strategy II should have better P-Q capability under low PCC voltages




Simulation Results

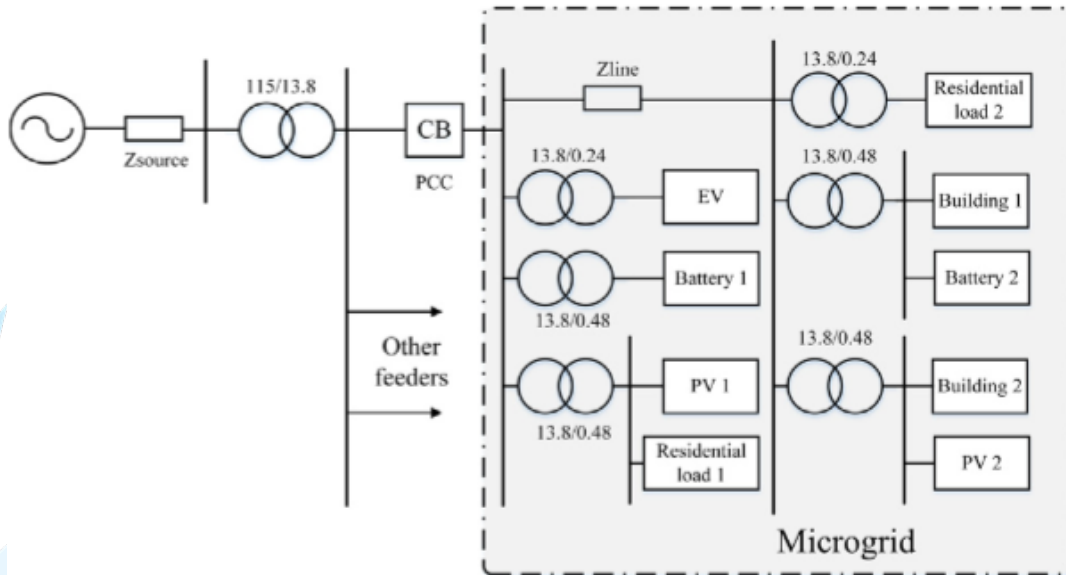- Microgrid: two GFM battery inverters, PVs grid-following, residential and commercial loads
- Simulation software: Matlab Simulink
- Events: grid-connected, unplanned islanding at 10 s, planned reconnection at 15 s, reconnect to the grid.



Unplanned islanding operation

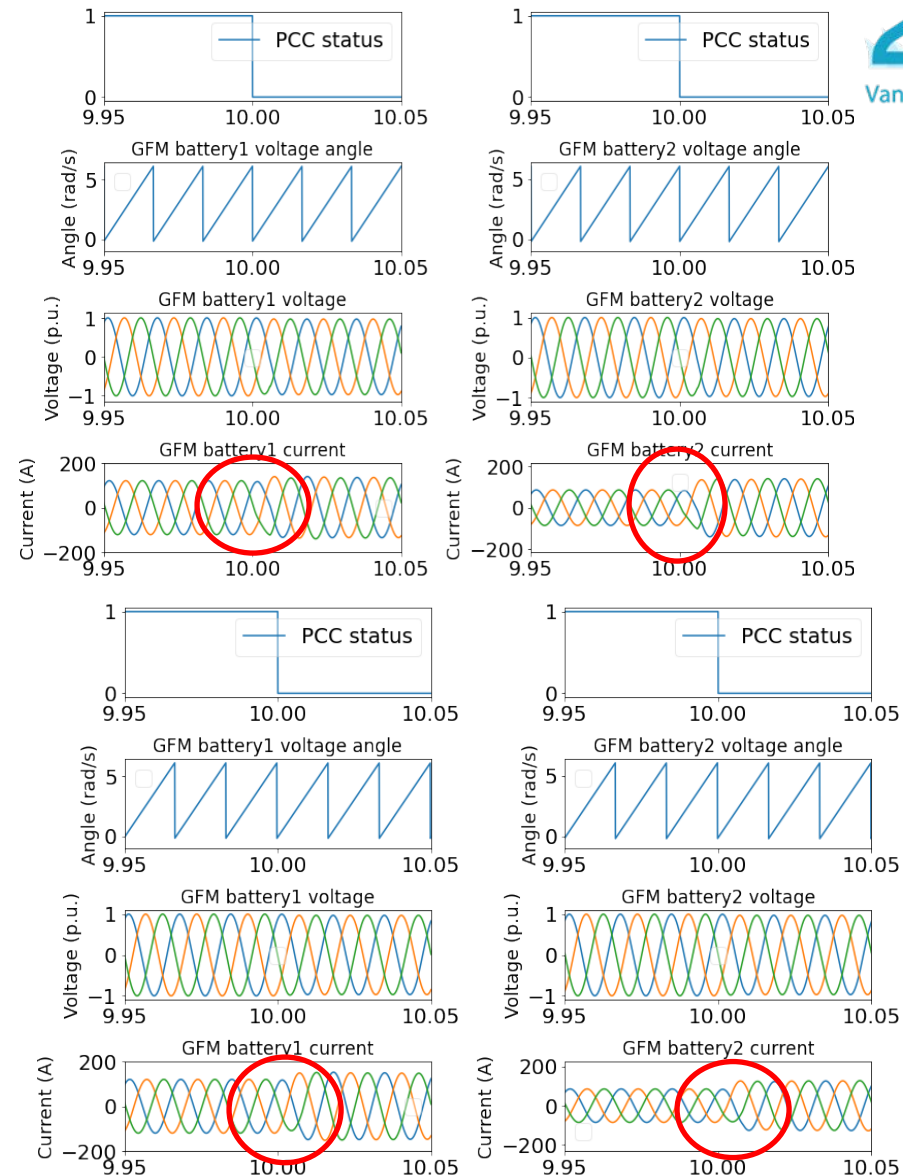

Strategy I

Strategy II

Simulation Results – Reconnection to the Grid




IEEE ENERGY CONVERSION CONGRESS & EXPO




Vancouver, Canada Oct. 10-14

Strategy I

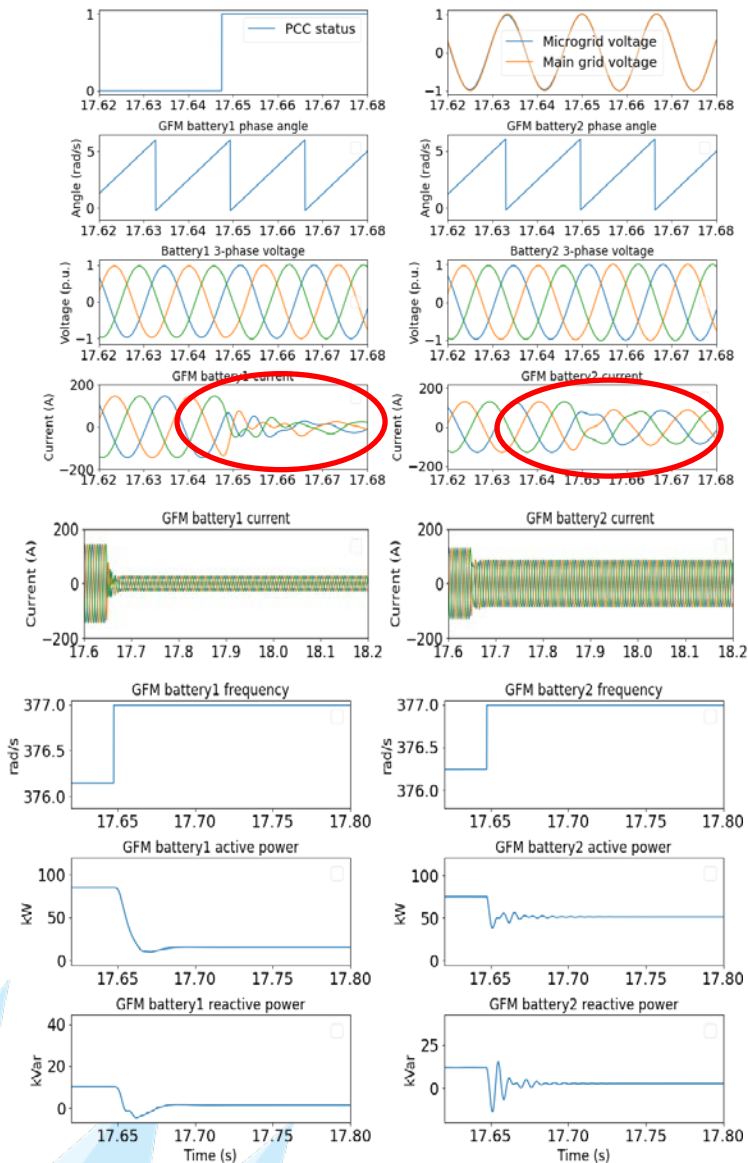


Strategy II


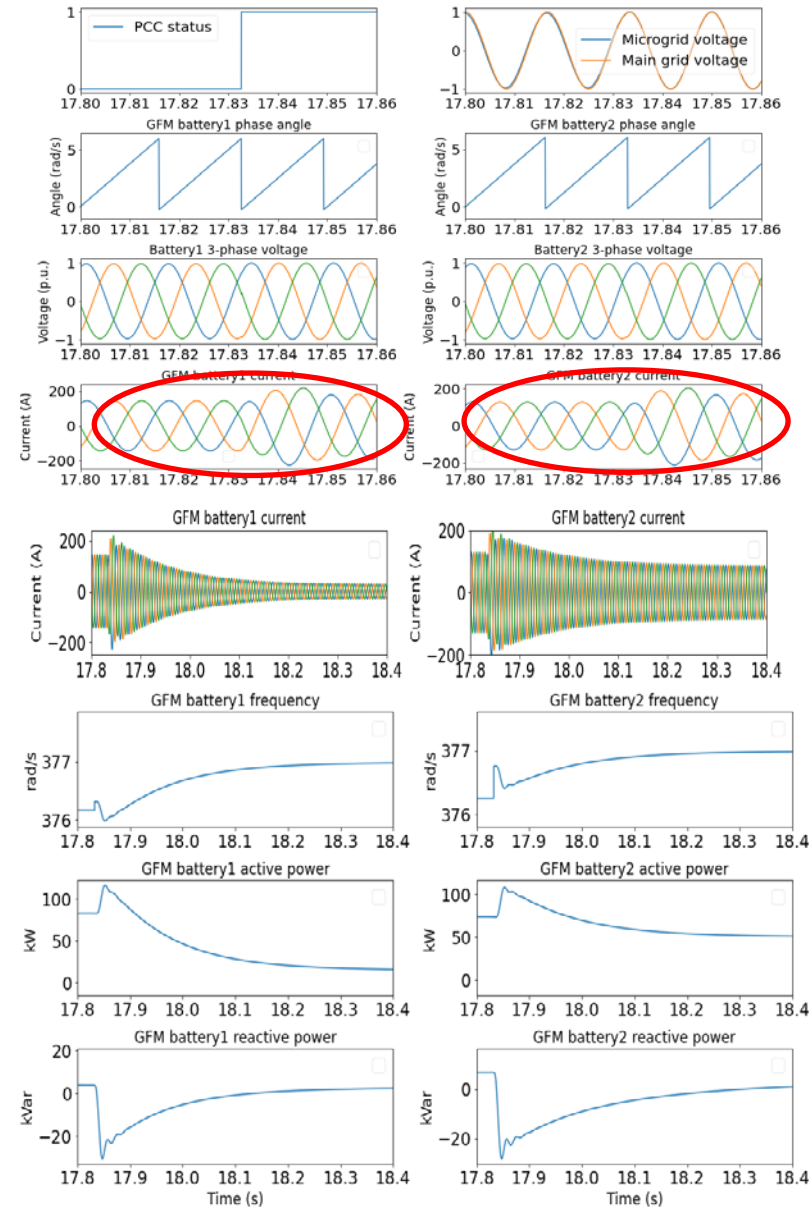


Simulation Results

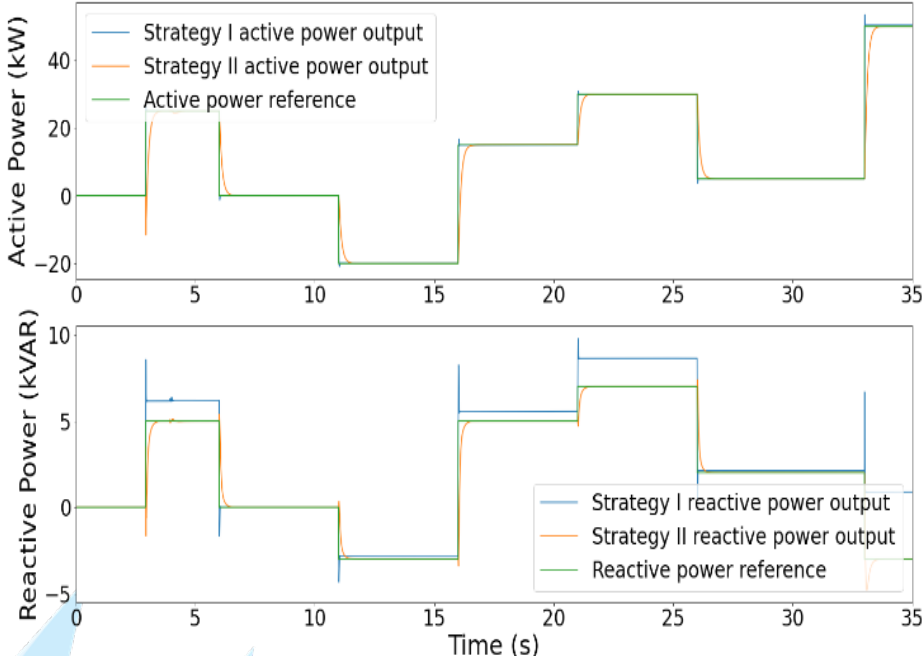- Power tracking performance in grid-connected mode



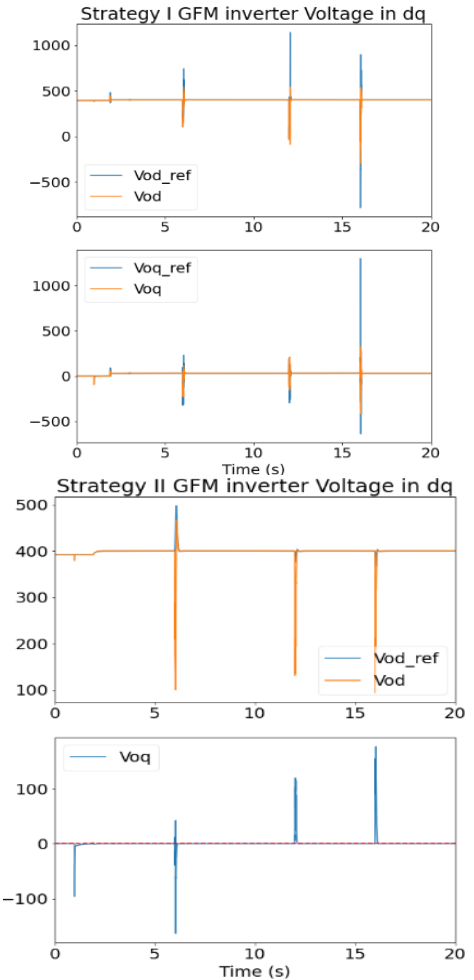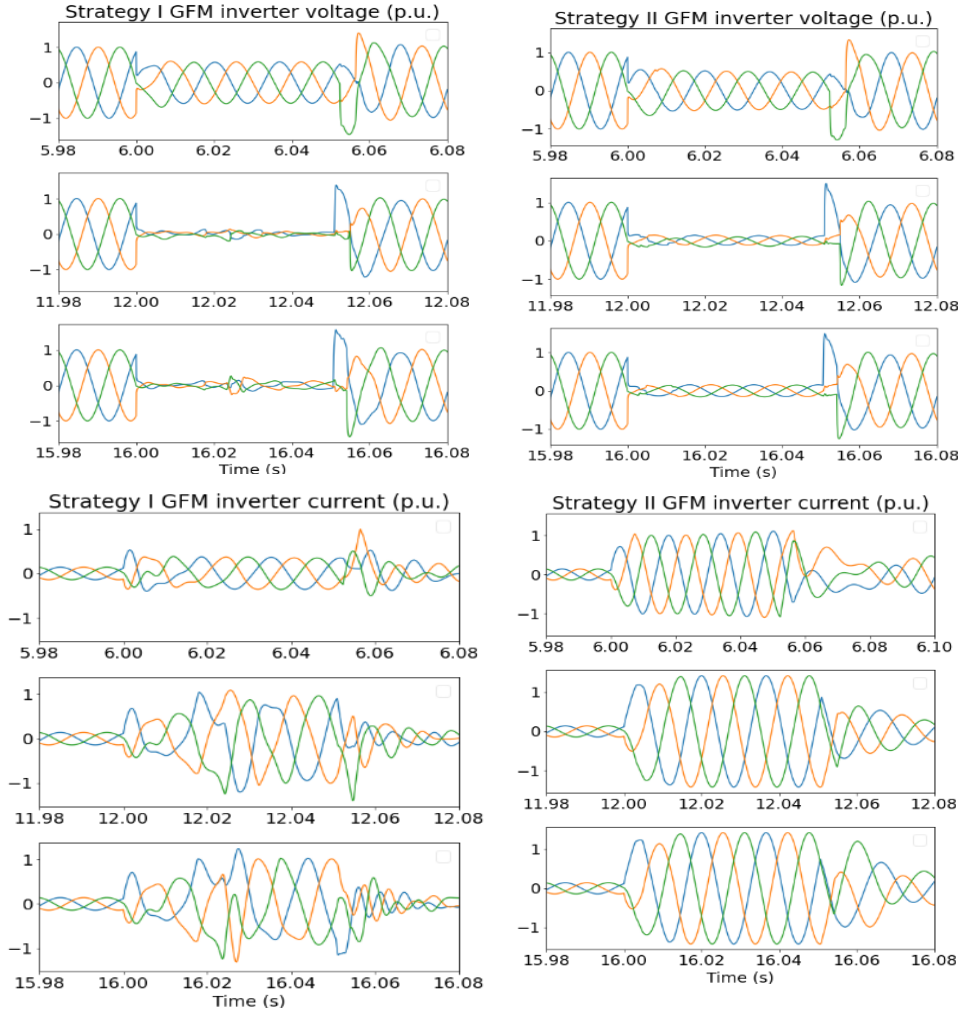- P-Q capability with low PCC voltages in grid-connected mode



Conclusion



| Circumstance | Strategy Comparison |
|-------------------------------------|--|
| Unplanned islanding | Both have smooth transients. Strategy II has slightly better transients in the output current. |
| Reconnection operation | Strategy I has better transients in frequency, output current, and power. |
| Power tracking | Strategy I reaches steady state faster with overshoots and has a tracking error in the reactive power. Strategy II has good tracking performance for both active and reactive power with an acceptable settling time. |
| P-Q capability with low PCC voltage | The low PCC voltage has a larger impact for Strategy I because its power control loop is a current control loop, and the current references depend on the PCC voltage. Strategy II has a larger P-Q capability with low PCC voltages and can maintain stability during fault ride-through. Strategy I can maintain stability only when the voltage is not less than a certain level. |

- Overall, Strategy II is recommended for microgrid applications
 - Comparable transition operation performance
 - Better power tracking in grid-connected mode
 - Better P-Q capability under faults or low PCC voltages
 - Easy for implementation.

This work was authored by the National Renewable Energy Laboratory, operated by Alliance for Sustainable Energy, LLC, for the U.S. Department of Energy (DOE) under Contract No. DE-AC36-08GO28308. Funding was provided by the U.S. DOE’s Solar Technology Energy Office (SETO) program. The views expressed in the article do not necessarily represent the views of the DOE or the U.S. Government. The U.S. Government retains and the publisher, by accepting the article for publication, acknowledges that the U.S. Government retains a nonexclusive, paid-up, irrevocable, worldwide license to publish or reproduce the published form of this work, or allow others to do so, for U.S. Government purposes.